

THE UNIVERSITY OF BRITISH COLUMBIA



ELECTRONICS II

ELEC 301

---

## MINI PROJECT 2

---

AUTHOR: TRAVIS INNES

STUDENT NUMBER: 28564383

PREPARED FOR: DR. NICOLAS JAEGER

March 3rd, 2024

# Contents

<b>1 Objectives</b>	<b>2</b>
<b>2 Part I: Methods of Simulating DC Operating Point</b>	<b>2</b>
2.a 2N2222A Small Signal Parameters from Datasheet . . . . .	2
2.b Comparing Simulation to Datasheet . . . . .	2
2.b.1 Plotting for $I_b$ vs $V_{BE}$ . . . . .	2
2.b.2 Plotting for $I_c$ vs $V_{CE}$ . . . . .	3
2.b.3 Plotting for $I_c$ vs $V_{CE}$ . . . . .	3
2.b.4 Bringing it together . . . . .	4
2.c Finding The DC Operating Point . . . . .	4
2.c.1 Using Simulated Paramters From Above . . . . .	5
2.c.2 Using 1/3 Rule . . . . .	5
2.c.3 Using 1/3 Rule and Available Resistors . . . . .	5
2.c.4 Comparing the 3 Methods . . . . .	6
2.d DC Operating Points of Alternate Transistors . . . . .	6
<b>3 Part II: The Common Emitter (CE) Amplifier</b>	<b>7</b>
3.a Calculating vs Approximation Methods: Comparing Poles/Zeros . . . . .	7
3.b Locating When Our Amplifier Goes Non-Liner . . . . .	11
3.c Input/Output Impedance at Midband . . . . .	11
3.d Selecting a Transistor . . . . .	12
<b>4 Part III: The Common Base (CB) Amplifier</b>	<b>12</b>
4.a Calculating vs Approximation Methods: Comparing Poles/Zeros . . . . .	12
4.b Locating When Our Amplifier Goes Non-Liner . . . . .	14
4.c Input/Output Impedance at Midband . . . . .	15
<b>5 Conclusion</b>	<b>15</b>
<b>6 Appendix</b>	<b>16</b>

# 1 Objectives

To develop familiarity with the transistor's hybrid-pi model and issues surrounding the biasing of transistors as well as to analyse and measure the characteristics of an important transistor amplifier using 3 commonly available transistors.

## 2 Part I: Methods of Simulating DC Operating Point

### 2.a 2N2222A Small Signal Parameters from Datasheet

Extracting the small signal h-parameters for 2N2222A at  $V_{CE} = 10V$ ,  $I_C = 1mA$ ,  $f = 1kHz$ , and  $T = 25C$ . Taken from 2N2222A datasheet.

H-Parameters	Min	Max
$H_{fe}$ (Small Signal Current Gain $\beta$ )	50	300
$H_{ie}$ (Input Impedance $r_\pi$ )	$2k\Omega$	$8k\Omega$
$H_{oe}$ (Output Admittance $1/r_o$ )	$5\mu S$	$35\mu S$

Table 2.1: Small Signal H-Parameters

### 2.b Comparing Simulation to Datasheet

Below we will simulate and graph the response of the 2N2222A. We will deduce variables  $g_m$ ,  $R_\pi$ ,  $\beta$ ,  $r_o$ , and  $V_A$  given  $I_b = 1mA$  and  $V_{CE} = 5V$  and compare it to the expected output from Table 2.1.

#### 2.b.1 Plotting for $I_b$ vs $V_{BE}$

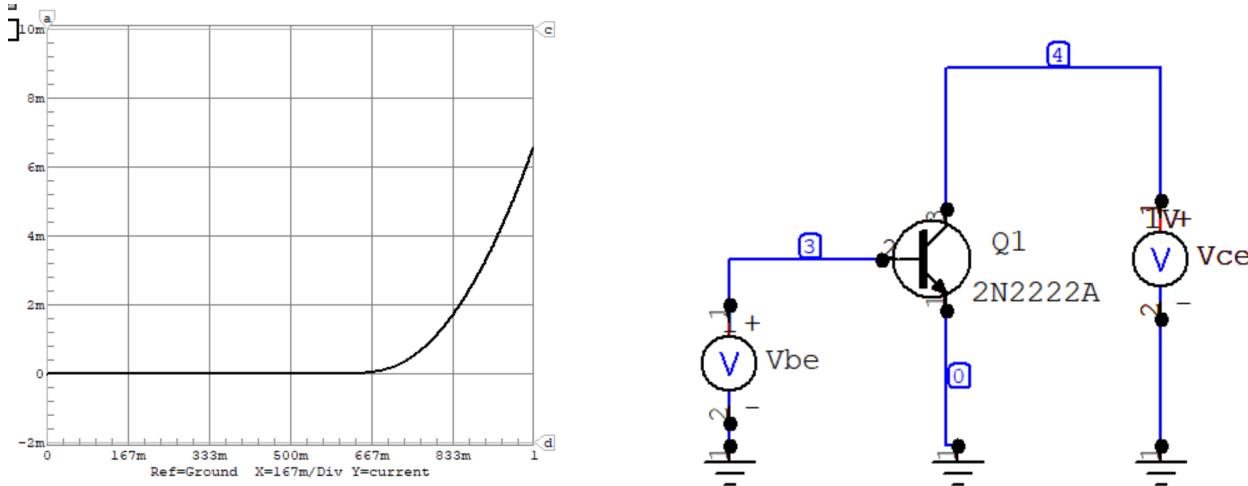


Figure 2.1:  $I_b$  vs  $V_{BE}$

### 2.b.2 Plotting for $I_c$ vs $V_{CE}$

The graph below shows a DC sweep on  $V_{CE}$  from 0-10V in increments of 10mV and will help us find Beta. From the data sheet we know beta is anywhere from 50-300, knowing a beta of 100 is common we will use that to center our  $I_B$  parameter on. When beta is 100  $I_B$  is 10uA. So we will sweep from 5uA-15uA in increments of 1uA. Below we can see at 5V and 1mA we center on our 2nd  $I_B$  sweep which corresponds to  $I_B = 6\text{uA}$ .

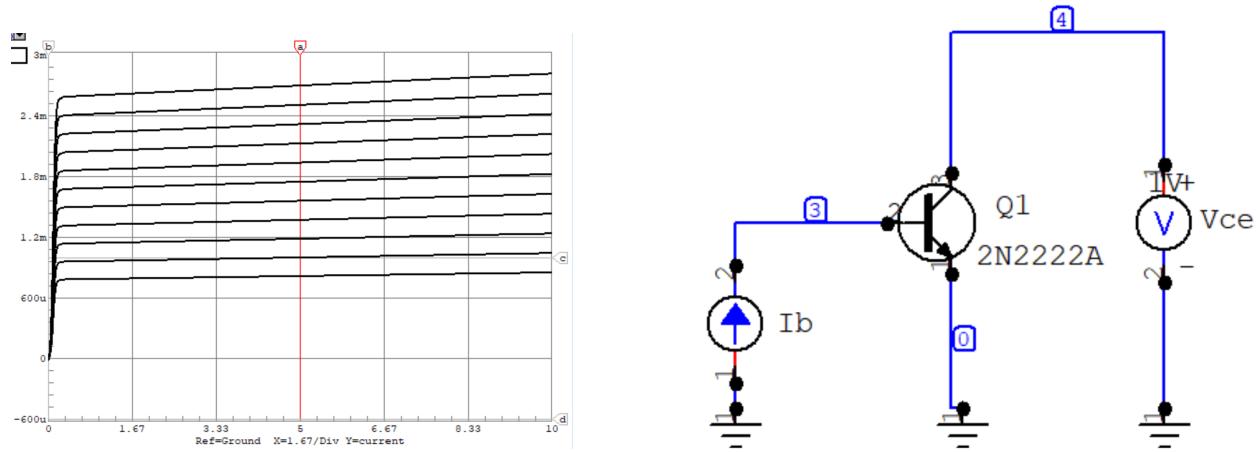


Figure 2.2:  $I_c$  vs  $V_{CE}$  with  $I_B$  as the variable parameter

### 2.b.3 Plotting for $I_c$ vs $V_{CE}$

The graph below shows a DC sweep on  $V_{CE}$  from 0-10V in increments of 10mV, and  $V_{BE}$  from 0.6-0.7V in increments of 10mV.

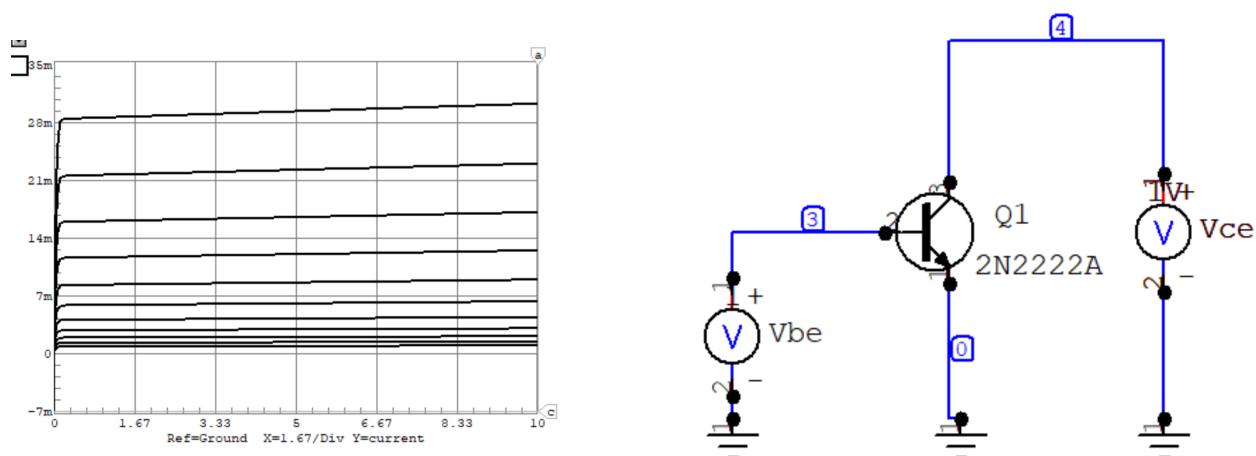


Figure 2.3:  $I_c$  vs  $V_{CE}$  with  $V_{BE}$  as the variable parameter

### 2.b.4 Bringing it together

Given from  $I_C = 1\text{mA}$ ,  $V_{CE} = 5\text{V}$ , and from Figure 2.2 where we conclude  $I_B$

$$g_m = \frac{I_C}{V_T} = \frac{1\text{mA}}{25\text{mV}} = [0.04\text{S}] \quad r_\pi = \frac{\beta}{g_m} = \frac{166.67}{0.04\text{S}} = [4.17\text{k}] \quad \beta = \frac{I_C}{I_B} = \frac{1\text{mA}}{6\mu\text{A}} = [166.67]$$

From Figure 2.3 can we extrapolate the Early voltage  $V_A$  from the graph by using the existing slope and derive  $r_o$ .

$$y = m * x + b \rightarrow 0 = \frac{1.681m}{9.214} * V_A + 28.42m \rightarrow V_A = [155.78]$$

$$r_o = \frac{V_A}{I_C} = \frac{155.78}{1\text{mA}} = [155.78\text{k}\Omega] \quad \frac{1}{r_o} = \frac{1}{155.78\text{k}\Omega} = [6.41\mu\text{S}]$$

Comparing our simulated values to our Datasheet values:

H-Parameters	Min	Max	Simulated
$H_{fe}$ (Small Signal Current Gain $\beta$ )	50	300	166.67
$H_{ie}$ (Input Impedance $r_\pi$ )	2k $\Omega$	8k $\Omega$	4.17k $\Omega$
$H_{oe}$ (Output Admittance $1/r_o$ )	5 $\mu\text{S}$	35 $\mu\text{S}$	6.41 $\mu\text{S}$

Table 2.2: Small Signal H-Parameters vs Simulated Parameters

Given our values fall between the expected min/max we see that they are reasonable. We now have extracted usable parameters which we can use to find our DC operating point.

### 2.c Finding The DC Operating Point

We use 3 different methods below to solve the bias circuit in Figure 2.4 to find the DC operating point. Firstly, we will solve for  $R_{B1}$ ,  $R_{B2}$ ,  $R_C$ , and  $R_E$  given we know  $V_{CC} = 15\text{V}$  and  $I_C = 1\text{mA}$ . Then find and compare DC operating points.

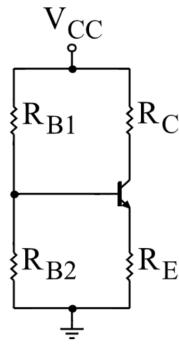


Figure 2.4: Simple Bias Network Circuit

### 2.c.1 Using Simulated Parameters From Above

From our simulated parameters above we know  $I_C$  and  $I_E$ . For the 2N2222A transistor to bias we want a  $V_{CE}$  of 4V or less and for  $R_E = R_C/2$ . So we can solve for  $R_E$  and  $R_C$ .

$$V_{CC} = (2 * R_E) * I_C + 4V + R_E * I_E \rightarrow [R_E = 3.67k\Omega] [R_C = 7.33k\Omega]$$

Transforming our bias circuit into a single mesh we can use the following equations to solve for  $R_{B1}$  and  $R_{B2}$ .

$$(\text{eq.1}) V_{BB} = I_B * R_{BB} + V_{BE} + R_E * I_E \rightarrow V_{CC} * \frac{R_{B2}}{R_{B2} + R_{B1}} = I_B * \frac{R_{B2}}{R_{B2} + R_{B1}} + 0.7 + R_E * I_E$$

$$(\text{eq.2}) I_2 = I_1 + I_B \rightarrow \frac{R_E * I_E + 0.7}{R_{B2}} = \frac{V_{CC} - V_B}{R_{B1}} - I_B$$

Solving the system of equations eq.1 and eq.2 find that the resistors  $R_{B1} : R_{B2}$  are related by a ratio of 1:0.41.  $[R_{B1} : R_{B2} = 1:0.41]$ . We will use this when we compare the three methods to choose a pair of resistors that make sense given we want a VBE below 4V.

### 2.c.2 Using 1/3 Rule

I will use the second method of the 1/3 rule. We know  $I_C$ ,  $V_{CC}$ ,  $V_B$ ,  $V_C$ ,  $V_E$ ,  $\beta$ , and  $I_1$  so we can immediately solve for  $R_C$ ,  $R_E$ ,  $R_{B1}$ , and  $R_{B2}$ .

$$R_C = \frac{V_{CC} - V_C}{I_C} = \frac{5V}{1mA} = [5k\Omega] \quad R_E = \frac{V_E}{I_E} = \frac{5V}{1mA} = [5k\Omega]$$

$$I_1 = \frac{I_C}{\sqrt{(\beta)}} = \frac{1mA}{\sqrt{166.67}} = 77.62uA \quad I_2 = I_1 - I_B = 77.62uA - \frac{1mA}{166.67} = 71.59uA$$

$$R_{B1} = \frac{V_{CC} - V_B}{I_1} = \frac{15 - 5.7}{77.62uA} = [119.82k\Omega] \quad R_{B2} = \frac{V_B}{I_2} = \frac{5.7}{71.59uA} = [79.62k\Omega]$$

### 2.c.3 Using 1/3 Rule and Available Resistors

The closest standard resistors for  $R_C$ ,  $R_E$ ,  $R_{B1}$ , and  $R_{B2}$  based on our calculated values.

$$5k\Omega \rightarrow [5.1k\Omega] \quad 119.82k\Omega \rightarrow [120k\Omega] \quad 79.62k\Omega \rightarrow [82k\Omega]$$

## 2.c.4 Comparing the 3 Methods

Using our resistances found from simulating as well our resistances found from using the 1/3 rule we can find and compare our estimated DC operating points for the given methods. Recalling back to 2.c.1 we deduced a relationship between  $R_{B1}$  and  $R_{B2}$ , namely  $R_{B1} : R_{B2} = 1:0.41$ . I have used 10k and 4.1k which keeps our transistor biased.

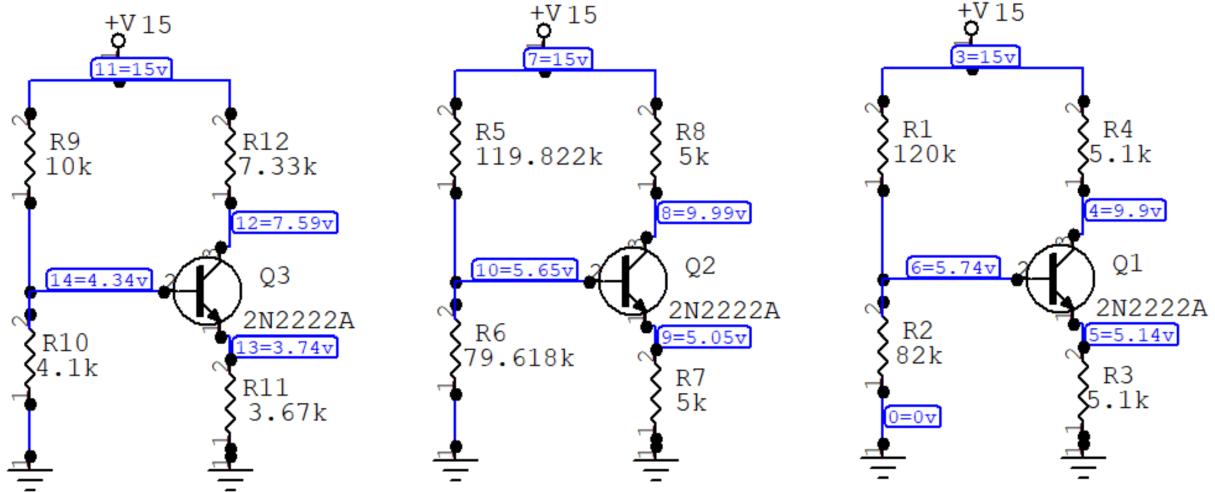


Figure 2.5: Simple Bias DC Operating Points

Methods	$V_C$	$V_B$	$V_E$	$I_C$	$I_B$	$I_E$
Simulation	7.59V	4.34V	3.74V	1.01mA	6.11uA	1.02mA
1/3 Rule	9.99V	5.65V	5.05V	1.00mA	6.05uA	1.01mA
1/3 Rule with Standard Resistances	9.90V	5.74V	5.14V	1.00mA	6.03uA	1.01mA

Table 2.3: Simple Bias DC Operating Points

We see that all methods are successful at biasing the transistor. Specifically going from the 1/3 rule to the 1/3 with standard resistors, we see the difference is negligible so it should always be a safe bet to use standard resistors. All methods see nearly the same currents through the transistor with slightly varying voltages

## 2.d DC Operating Points of Alternate Transistors

To check the robustness of our 2.c.3 solution we will compare the result when applied to other transistors. Here we compare 2N2222A with 2N3904 and 2N4401. What we find is nearly identical results for their DC operating points. There is however a noticeable change in  $V_{BE}$  drop. 2N2222A with a  $V_{BE}$  of 0.6V, 2N3904 with a  $V_{BE}$  of 0.65V, 2N4401 with a  $V_{BE}$  of 0.75V.

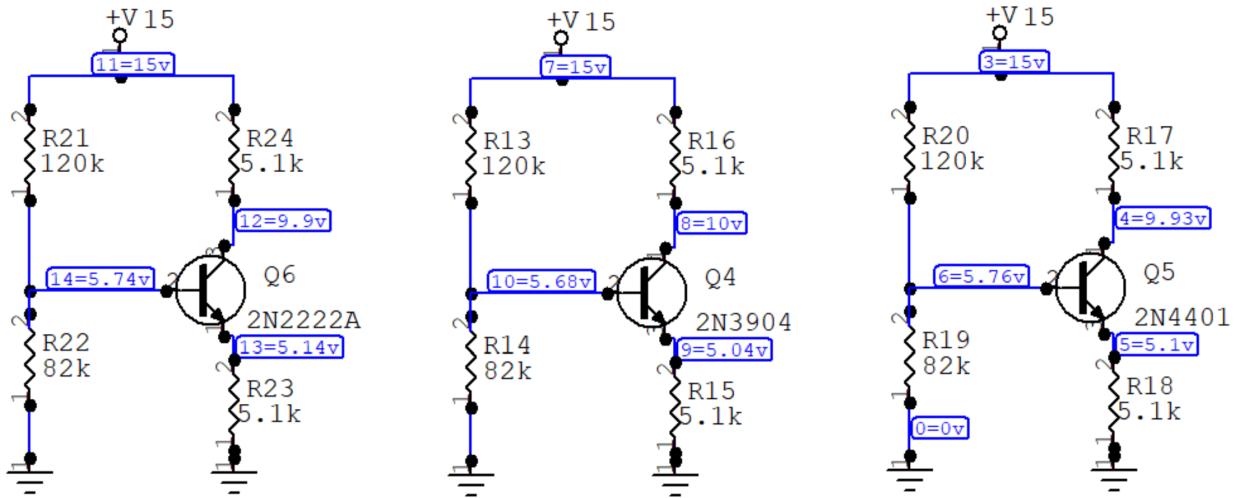


Figure 2.6: Simple Bias DC Operating Points: Differing Transistors

Transistors: Using Method from 2.c.3	$V_C$	$V_B$	$V_E$	$I_C$	$I_B$	$I_E$
2N2222A	9.90V	5.74V	5.14V	1.00mA	6.03uA	1.01mA
2N3904	10.00V	5.68V	5.04V	0.99mA	5.93uA	0.99mA
2N4401	9.93V	5.76V	5.10V	0.99mA	5.98uA	1.00mA

Table 2.4: Simple Bias DC Operating Points: Differing Transistors

### 3 Part II: The Common Emitter (CE) Amplifier

#### 3.a Calculating vs Approximation Methods: Comparing Poles/Zeros

APPROXIMATION METHOD:

First we simulate and approximate the differences using both 2N4401 and 2N3904.

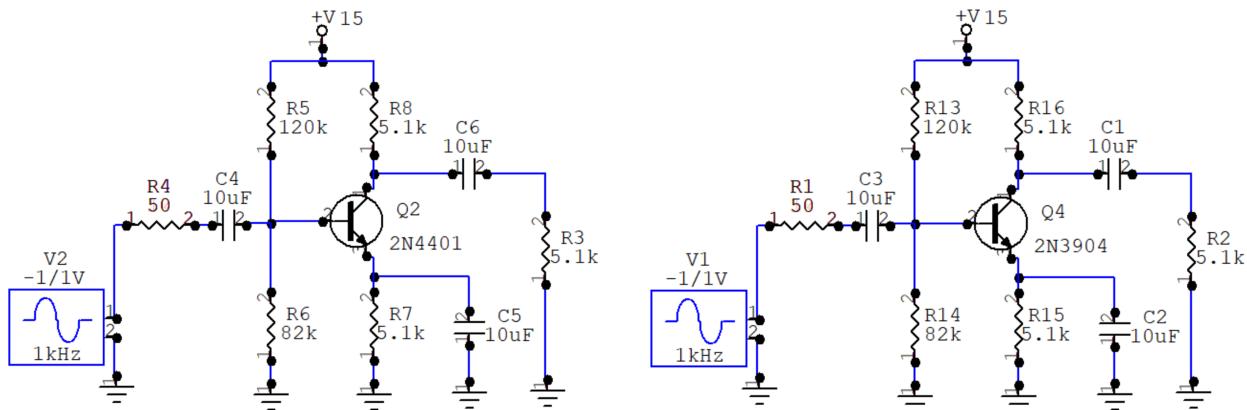


Figure 3.1: 2N4401 (left) and 2N3904 (right) CE Amplifier

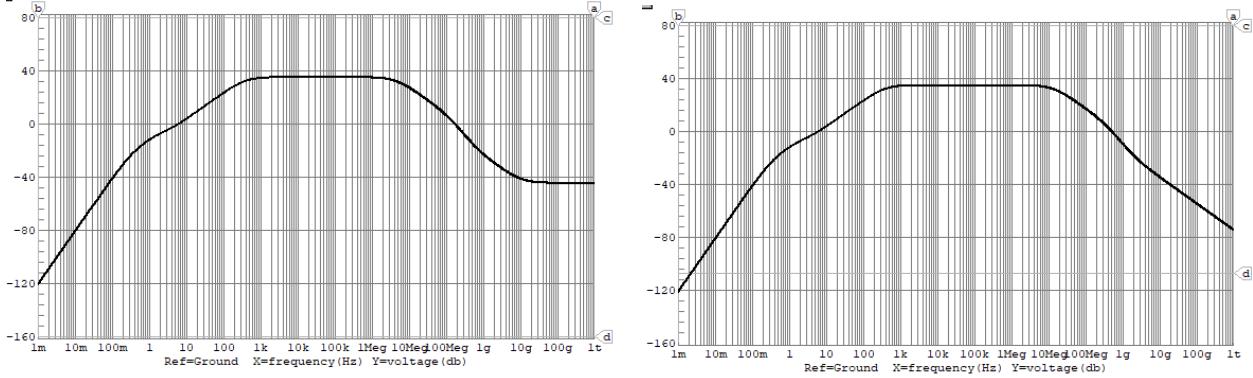


Figure 3.2: 2N4401 (left) and 2N3904 (right) CE Amplifier Bode Magnitude Plots

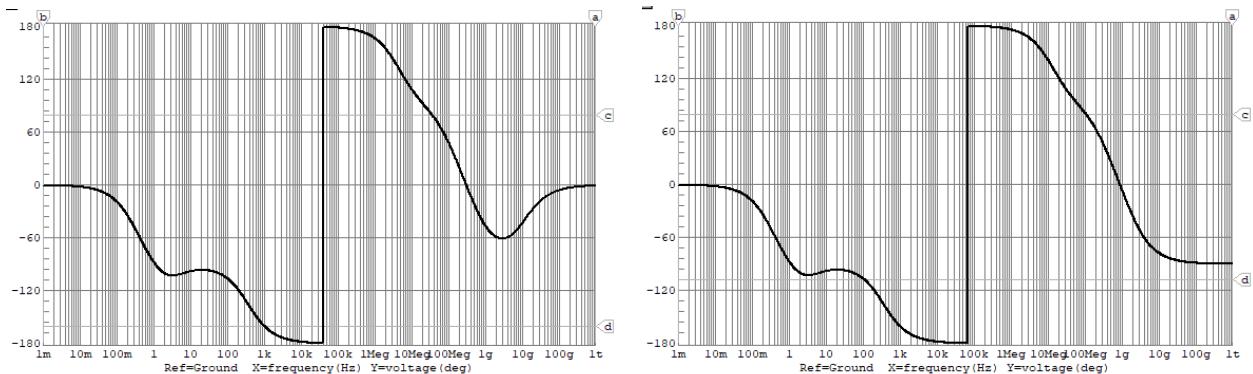


Figure 3.3: 2N4401 (left) and 2N3904 (right) CE Amplifier Bode Phase Plots

We can approximate the poles using the Bode magnitude graphs in Figure 3.2:

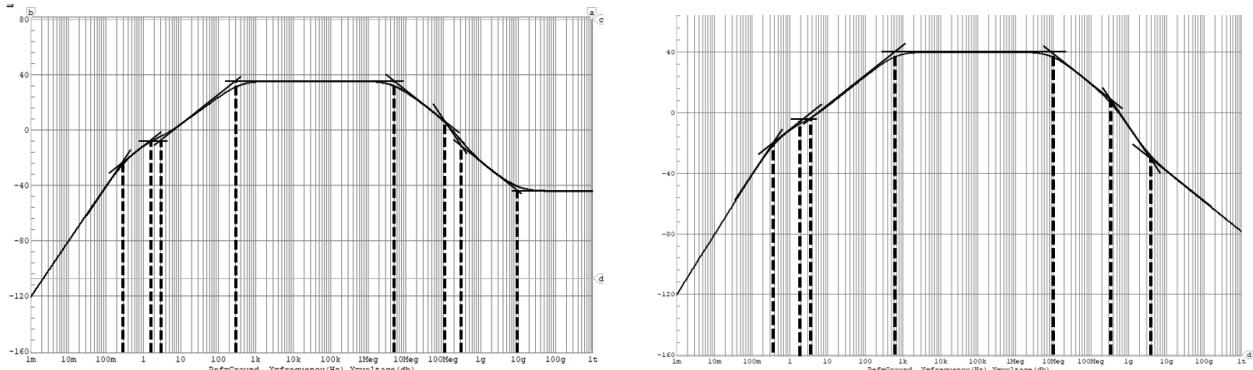


Figure 3.4: 2N4401 (left) and 2N3904 (right) Approximated Poles/Zeros

Transistor	$\omega_{LP1}$	$\omega_{LP2}$	$\omega_{LP3}$	$\omega_{HP1}$	$\omega_{HP2}$	$\omega_{ZL1-2}$	$\omega_{ZL3}$	$\omega_{ZH1}$	$\omega_{ZH2}$
2N4401	0.29Hz	1.69Hz	0.35kHz	98.1MHz	4.89MHz	0	3.11Hz	0.2GHz	9.9GHz
2N3904	0.36Hz	1.73Hz	0.67kHz	278MHz	10.1MHz	0	3.30Hz	3.9GHz	$\infty$

Table 3.1: Simulated and Approximated Poles/Zeros

## CALCULATION METHOD:

Now we will calculate the locations of the poles and zeros using Miller's Theorem and OC/SC time constants and compare them to the simulated + approximated poles/zeros.

We will use our small signal model and convert 2N4401 and 2N3904 into equivalent circuits. Calculating  $C_\pi$  and  $C_\mu$  for our small signal model starting with 2N3904:

$$g_m = \frac{I_C}{V_T} = \frac{0.99mA}{25mV} = \boxed{0.0396} \quad V_{CB} = V_C - V_B = \boxed{4.83V} \quad r_\pi = \frac{\beta}{g_m} = \frac{167}{0.0396} = \boxed{4.17k}$$

$$C_{\pi} = 2 * CJE + TF * g_m = 2 * 4.5pF + 400pF * 0.0396 = 24.84pF$$

$$C_\mu = \frac{CJC}{(1 + \frac{V_{CB}}{VJC})^{MJC}} = \frac{4pF}{(1 + \frac{4.83V}{750m})^{330m}} = \boxed{2.06pF}$$

Applying those values to the small signal model circuit:

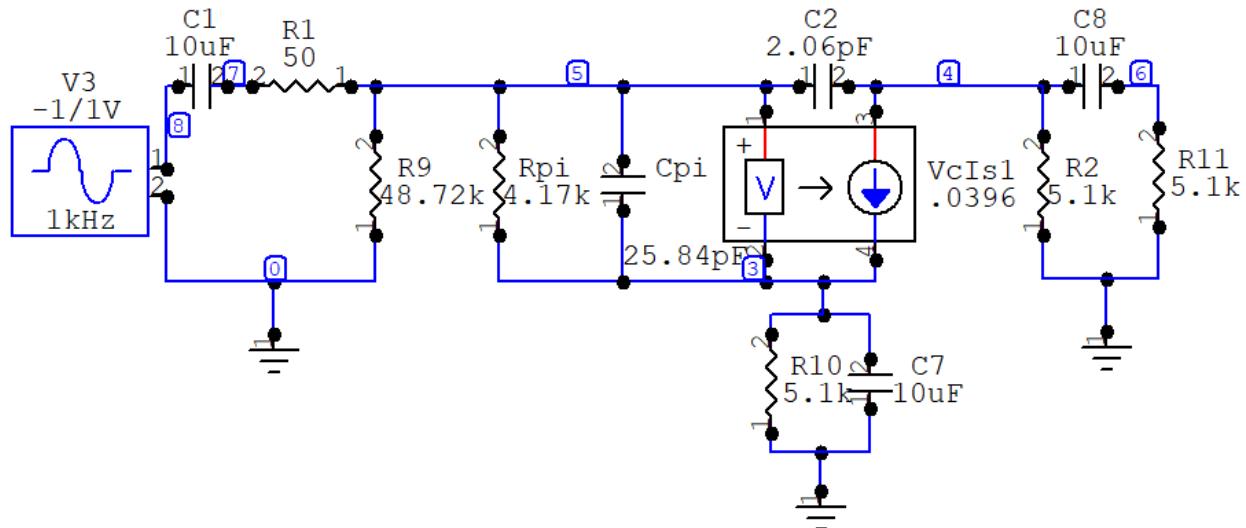


Figure 3.5: Small Signal Model of 2N3904:

Calculating Miller's for the high frequency circuit for 2N3904:

$$k = \boxed{-100} \quad C_{\mu 1} = C_{\mu} * (1 - k) = \boxed{208 \text{pF}} \quad C_{\mu 2} = C_{\mu} * (1 - \frac{1}{k}) = \boxed{2.08 \text{pF}}$$

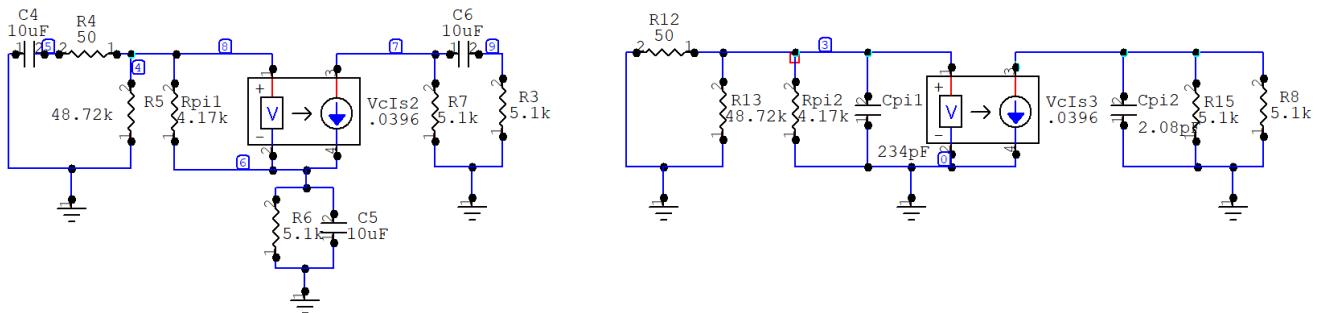


Figure 3.6 Low (left) and High (right) Frequency Small Signal Model:

Calculating Poles from high and low frequency circuits from Figure 3.6

$$\omega_{LP1}^{SC} = \frac{2\pi}{10uF*(50+48.72k||(\beta*(4.17k+5.1k)))} = \boxed{0.35\text{Hz}} \quad \omega_{HP1}^{SC} = \frac{1}{2.08pF*5.1k||5.1k} = \boxed{30.01\text{MHz}}$$

$$\omega_{LP2}^{SC} = \frac{2\pi}{10uF*(10.2k)} = \boxed{1.56\text{Hz}} \quad \omega_{HP2}^{SC} = \frac{1}{234pF*(48.7k||50||4.17k)} = \boxed{13.7\text{MHz}}$$

$$\omega_{LP3}^{SC} = \frac{2\pi}{10uF*((\frac{50}{\beta}||\frac{48.7k}{\beta}+\frac{4.17k}{\beta})||5.1k))} = \boxed{632.96\text{Hz}}$$

Zeros from high and low frequency circuits from Figure 3.6:

$$\omega_{LZ1} = \frac{2\pi}{5.1k*10uF} = \boxed{3.12\text{Hz}} \quad \text{With two zeros at 0 and one at } \infty$$

We will now preform the same series of calculations for 2N4401:

$$g_m = \frac{I_C}{V_T} = \frac{0.99mA}{25mV} = \boxed{0.0396} \quad V_{CB} = V_C - V_B = \boxed{4.17\text{V}} \quad r_\pi = \frac{\beta}{g_m} = \frac{167}{0.0396} = \boxed{4.17\text{k}}$$

$$C_\pi = 2 * CJE + TF * g_m = 2 * 23.4pF + 512pF * 0.0396 = \boxed{67.08\text{pF}}$$

$$C_\mu = \frac{CJC}{(1+\frac{V_{CB}}{V_{JC}})^{MJC}} = \frac{10.2pF}{(1+\frac{4.17V}{750m})^{330m}} = \boxed{5.48\text{pF}}$$

$$k = \boxed{-100} \quad C_{\mu 1} = C_\mu * (1 - k) = \boxed{553\text{pF}} \quad C_{\mu 2} = C_\mu * (1 - \frac{1}{k}) = \boxed{5.53\text{pF}}$$

$$\omega_{LP1}^{SC} = \frac{2\pi}{10uF*(50+48.72k||(\beta*(4.17k+5.1k)))} = \boxed{0.35\text{Hz}} \quad \omega_{HP1}^{SC} = \frac{1}{5.53pF*5.1k||5.1k} = \boxed{11.29\text{MHz}}$$

$$\omega_{LP2}^{SC} = \frac{2\pi}{10uF*(10.2k)} = \boxed{1.56\text{Hz}} \quad \omega_{HP2}^{SC} = \frac{1}{589pF*(48.7k||50||4.17k)} = \boxed{5.47\text{MHz}}$$

$$\omega_{LP3}^{SC} = \frac{2\pi}{10uF*((\frac{50}{\beta}||\frac{48.7k}{\beta}+\frac{4.17k}{\beta})||5.1k))} = \boxed{632.96\text{Hz}}$$

$$\omega_{LZ1} = \frac{2\pi}{5.1k*10uF} = \boxed{3.12\text{Hz}} \quad \text{With two zeros at 0 and one at } \infty$$

Below is the calculated (C) and approximated poles (A):

Transistor	$\omega_{LP1}$	$\omega_{LP2}$	$\omega_{LP3}$	$\omega_{HP1}$	$\omega_{HP2}$	$\omega_{ZL1-2}$	$\omega_{ZL3}$	$\omega_{ZH1}$	$\omega_{ZH2}$
2N4401(C)	0.35Hz	1.56Hz	0.63kHz	11.3MHz	5.47MHz	0	3.12Hz	$\infty$	$\infty$
2N3904(C)	0.35Hz	1.56Hz	0.63kHz	30.0MHz	13.7MHz	0	3.12Hz	$\infty$	$\infty$
2N4401(A)	0.29Hz	1.69Hz	0.35kHz	98.1MHz	4.89MHz	0	3.11Hz	0.2GHz	9.9GHz
2N3904(A)	0.36Hz	1.73Hz	0.67kHz	278MHz	10.1MHz	0	3.30Hz	3.9GHz	$\infty$

Table 3.2: Calculated (C) vs Approximated (A) Poles/Zeros

We see that the estimation is generally fairly close to the approximation, but breaks down in the high frequency. This is likely due to the close proximity of the poles. I used a linear approximation method, and generally the closer the calculated poles the less accurate the simulation + simulation is. We also get real zero values when we approximate versus our more undefined calculated values.

### 3.b Locating When Our Amplifier Goes Non-Liner

A circuit will start to become non-linear near it's 3dB frequency. I will use a midband frequency of 1kHz and peak of 100mV. We see both transistors go non-linear after around 65uV.

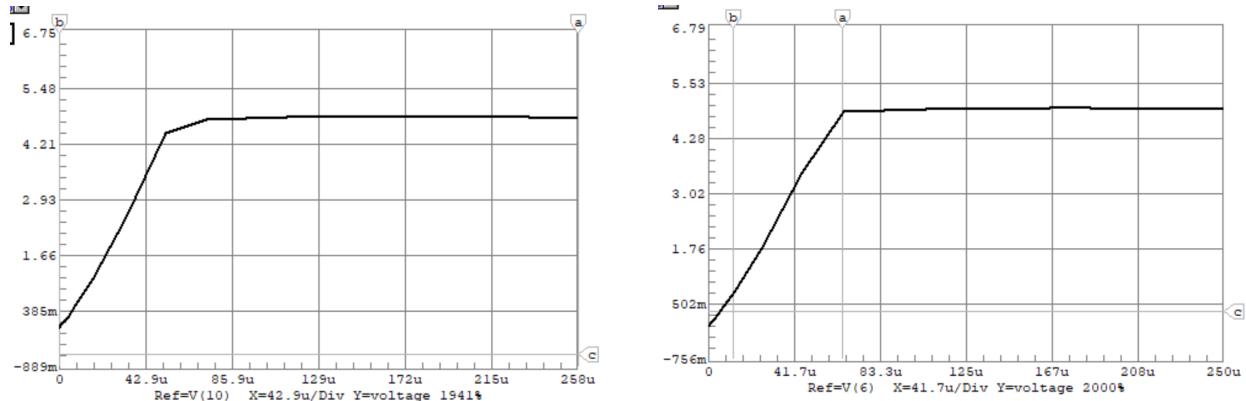


Figure 3.7: 2N4401 (left) and 2N3904 (right) Approximated Poles/Zeros

### 3.c Input/Output Impedance at Midband

Solving and simulating for input and output impedance:

$$Z_{input} = R_{BB} || r_{pi} \quad Z_{output} = R_C$$

Method	$Z_{input}$ (2N4401)	$Z_{Output}$ (2N4401)	$Z_{input}$ (2N3904)	$Z_{Output}$ (2N3904)
Simulated	$3.8k\Omega$	$5.1k\Omega$	$3.8k\Omega$	$5.1k\Omega$
Calculated	$3.8k\Omega$	$5.1k\Omega$	$3.8k\Omega$	$5.1k\Omega$

Table 3.3: Input/Output Impedance: Simualted+Approx and Calculated

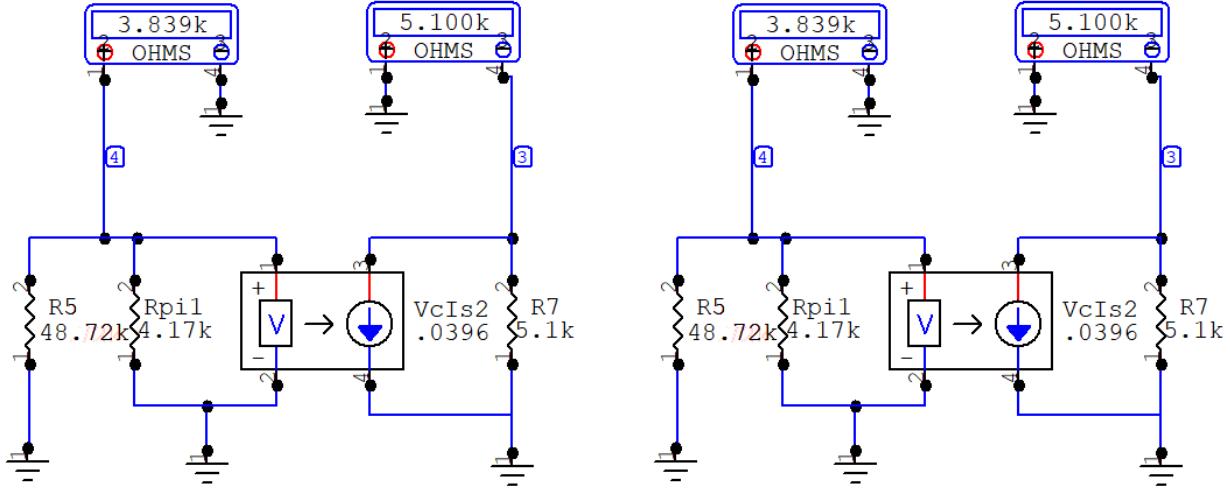


Figure 3.8: 2N4401 (left) and 2N3904 (right) Simulated Input/Output Impedance

### 3.d Selecting a Transistor

Both transistors are extremely similar. One of the differences are the pole locations. And, given that 2N3904 has a larger midband range I would pick it for more applications over 2N4401.

## 4 Part III: The Common Base (CB) Amplifier

### 4.a Calculating vs Approximation Methods: Comparing Poles/Zeros

APPROXIMATION METHOD:

We will now simulate and approximate 2N3904.

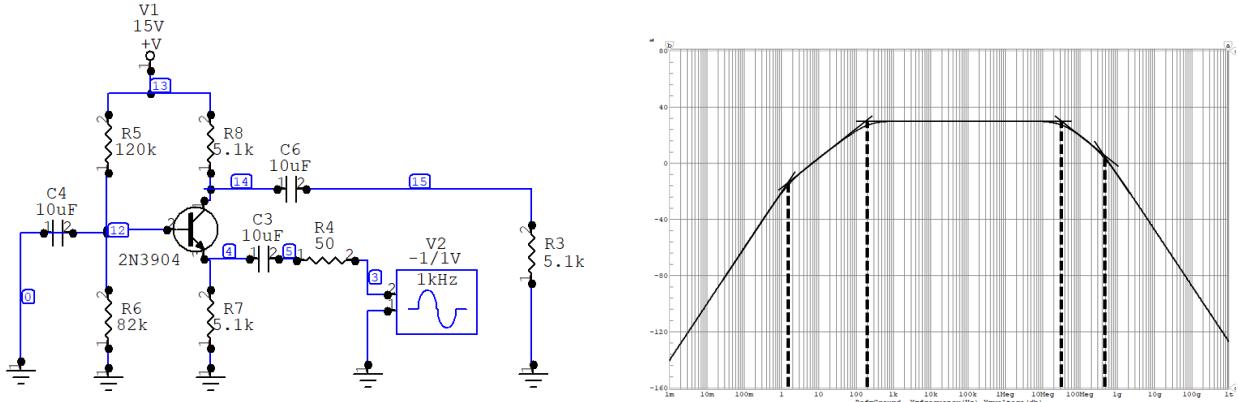


Figure 4.1: 2N3904 BE Amplifier and Corresponding Bode Response

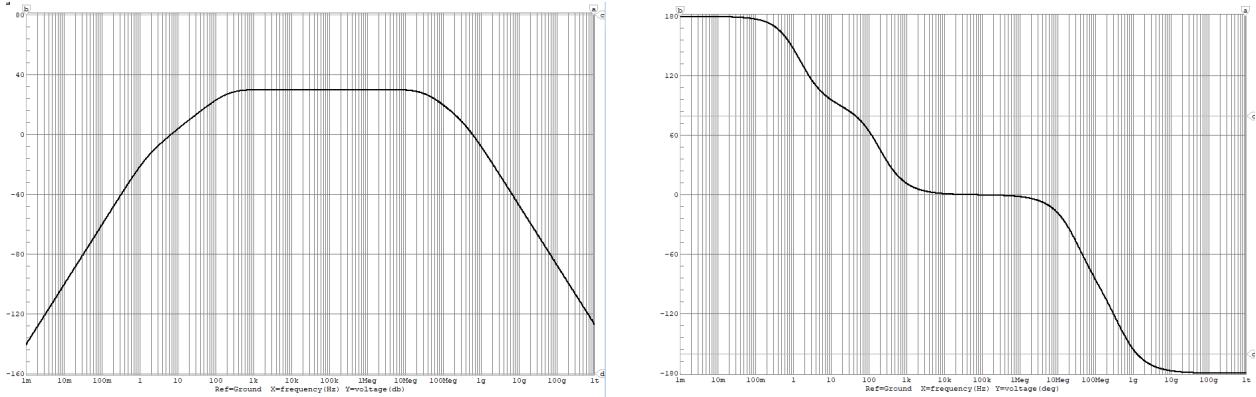


Figure 4.2: Bode Magnitude and Phase Responses

Transistor	$\omega_{LP1}$	$\omega_{LP2}$	$\omega_{HP1}$	$\omega_{HP2}$	$\omega_{ZL1}$	$\omega_{ZH1}$
2N3904	1.59Hz	171Hz	22.1MHz	30.6MHz	0	$\infty$

Table 4.1: Simulated and Approximated Poles/Zeros

#### CALCULATION METHOD:

Now we will calculate the locations of the poles and zeros using Miller's Theorem and OC/SC time constants and compare them to the simulated + approximated poles/zeros. We will use the small signal model values we found in 3.a to derive a circuit.

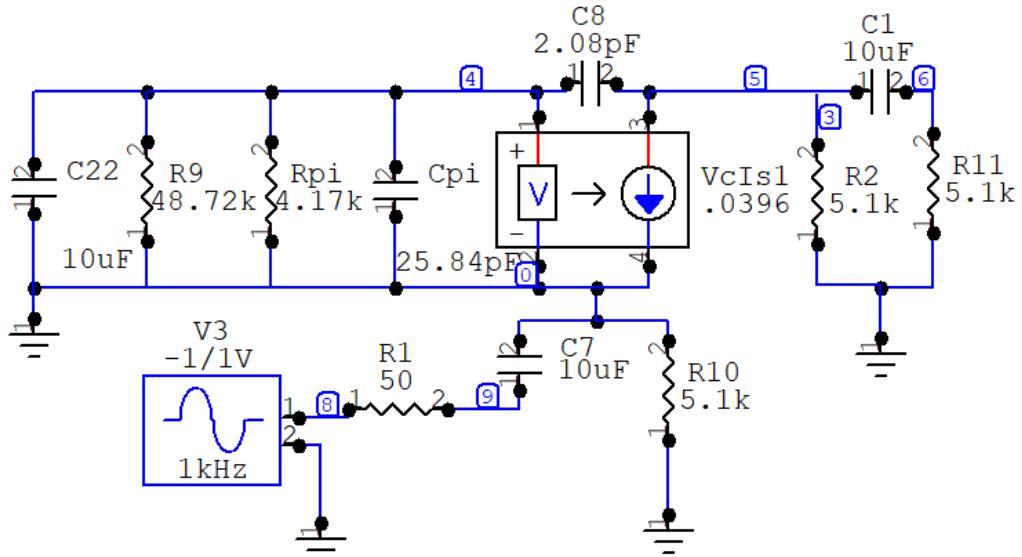


Figure 4.3: Small Signal Model of 2N3904

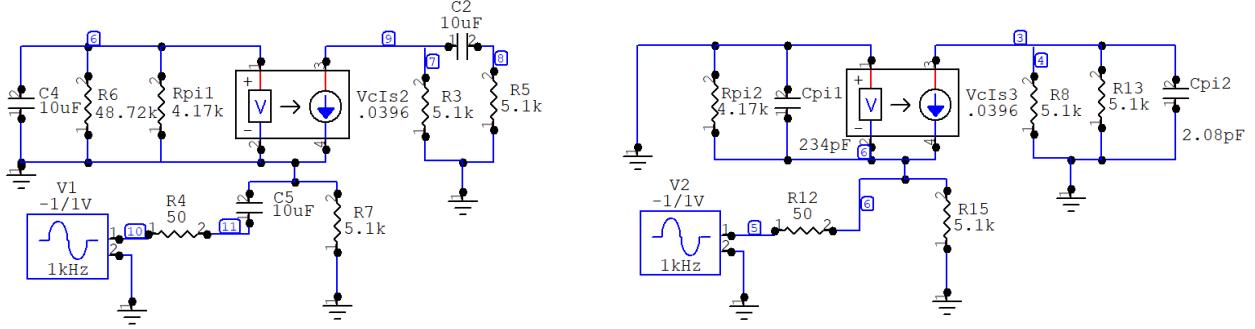


Figure 4.4: Low (left) and High (right) Frequency Small Signal Model

Calculating Poles from high and low frequency circuits from Figure 4.4

$$\omega_{LP1}^{SC} = \frac{2\pi}{10uF * (48.72k || (4.17k + \beta * 5.1k))} = [0.46\text{Hz}]$$

$$R_{test} = \frac{1}{r\pi} = \frac{2}{10k || 50} = 24.72\Omega$$

$$\omega_{LP2}^{SC} = \frac{2\pi}{10uF * (10.2k)} = [1.56\text{Hz}]$$

$$\omega_{HP1}^{SC} = \frac{1}{R_{test}C} = \frac{1}{24.72 * 10pF} = [27.5\text{MHz}]$$

$$\omega_{LP3}^{SC} = \frac{2\pi}{10uF * (\frac{4.17k}{\beta} + 50)} = [211.87\text{Hz}]$$

$$\omega_{HP2}^{SC} = \frac{1}{2pF * 5k} = [30.6\text{MHz}]$$

$$\omega_{LZ2}^{SC} = \frac{2\pi}{10uF * 48.72k} = [0.33\text{Hz}]$$

Transistor	$\omega_{LP1}$	$\omega_{LP2}$	$\omega_{LP3}$	$\omega_{HP1}$	$\omega_{HP2}$	$\omega_{ZL1}$	$\omega_{ZL2}$	$\omega_{ZH1}$
2N3904	0.46Hz	1.56Hz	211.87Hz	27.1MHz	439MHz	0	0.3	$\infty$

Table 4.2: Calculated Poles/Zeros

This is a very interesting result. We see that our calculated poles are very different compared to the poles we simulated and estimated. The extra pole/zero pair that we didn't anticipate are very close to each other, thus cancel out in the Bode plot. Additionally our estimates on the graph are off and our poles are actually calculated to be very close to each other. This is because the method of estimating we used, linear extrapolating, works poorly when poles are close together.

## 4.b Locating When Our Amplifier Goes Non-Liner

A circuit will start to become non-linear near it's 3dB frequency. I will use a midband frequency of 1kHz and peak of 1V. We see both transistors go non-linear after around 50uV.

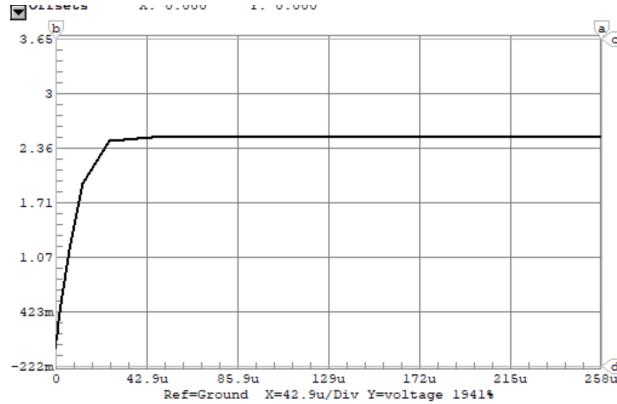


Figure 4.3: 2N3904 Going Non-Linear

#### 4.c Input/Output Impedance at Midband

$$Z_{input} = R_{BB} || r_{pi} \quad Z_{output} = R_C$$

Method	$Z_{input}$	$Z_{Output}$
Simulated	24.88Ω	5.1kΩ
Calculated	24.72Ω	5.1kΩ

Table 3.3: Input/Output Impedance: Simualted+Approx and Calculated

## 5 Conclusion

After analyzing different methods and measuring/simulating the behaviour of transistors we can see that our estimation methods such as the 1/3 rule and the small-signal model approximations work very well and can be used to attain accurate results.

## 6 Appendix

### References

- [1] <https://www.mouser.ca/datasheet/2/389/CD00003223-491114.pdf>
- [2] <https://www.youtube.com/watch?v=OrsAtjiChLkab> channel = SalimKoteish
- [3] <https://www.youtube.com/watch?v=F97vyRhyl8ab> channel = SimulateElectronics
- [4] <https://www.youtube.com/watch?v=y2eenHbFiF8ab> channel = APDahlen
- [5] <https://www.cxi1.co.uk/ltpice/dccircuits.htm>